



Civilittee
اللجنة الأكاديمية لقسم الهندسة المدنية
www.Civilittee.com

سكند

فيزياء 2

Physics 2



[civilittee.hu](https://www.instagram.com/civilittee.hu)



لجنة المدني | Civilittee HU



Civilittee Hashemite



www.civilittee.com

① سعة لحاية الاجهزة

② تخزين الطاقة الكهربائية

chapter (26)

Capactance and dielectrics

المواد العازلة ← العازل

↳ combination of 2 conductors called a (capacitor)

* capacitor (مكثف)

* capacitance (سعة)

• potential difference (ΔV)

• Capacitance: ratio between the magnitude of the charge (Q) on either conductor to the magnitude of potential difference between them.

$$C = \frac{|Q|}{|\Delta V|} = \left(\frac{C}{V} \right) \rightarrow \text{الوحدة} = \text{Farad (F)}$$


لغة الفلكس
ع

$$nF, \mu F, mF, PF$$

$10^{-9}, 10^{-6}, 10^{-3}, 10^{-12}$

① capacitance of an insulated charged sphere:
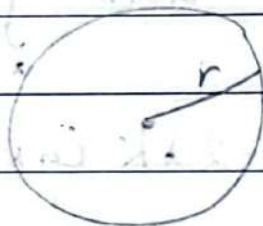
$$C = \frac{Q}{V} = \frac{Q}{\frac{k_e Q}{r}} = \frac{r}{k_e} = 4\pi\epsilon_0 r$$



$$C = 4\pi\epsilon_0 r = \frac{r}{k_e}$$

$$V = \frac{k_e Q}{r}$$

② parallel plates capacitor::


between them $E = \frac{\sigma}{\epsilon_0}$

$$\Delta V = Ed$$

$$\Delta V = \frac{\sigma d}{\epsilon_0}$$

$$C = \frac{Q}{\Delta V} = \frac{\sigma A}{\frac{\sigma d}{\epsilon_0}} = \frac{A \epsilon_0}{d}$$

$$C = \frac{A \epsilon_0}{d}$$

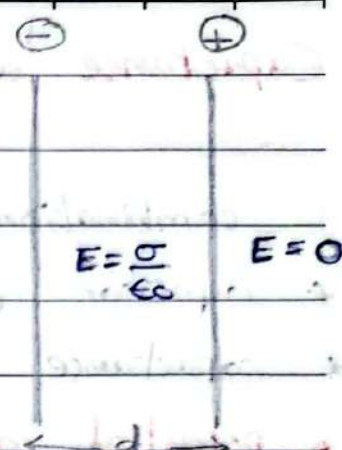

③ cylindrical capacitor:


$$\Delta V = - \int_a^b E \cdot ds$$

$$= -2\lambda K \int_a^b \frac{1}{r} dr$$

$$= -2\lambda K \ln r \Big|_a^b = -2\lambda K (\ln b - \ln a)$$

$$= -2\lambda K \ln\left(\frac{b}{a}\right) \#$$
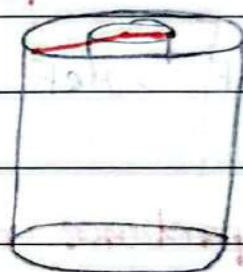
$$C = \frac{Q}{V} \rightarrow C = \frac{\lambda L}{2\lambda K \ln\left(\frac{b}{a}\right)}$$



$$C = \frac{L}{2K \ln\left(\frac{b}{a}\right)}, \therefore \frac{C}{L} = \frac{1}{2K \ln\left(\frac{b}{a}\right)}$$

per unit length

④ Spherical capacitor:


$$E = \frac{KQ}{r^2}$$

$$\Delta V = - \int_a^b E \cdot ds$$

$$= -KQ \int_a^b \frac{1}{r^2} dr = \left[\frac{KQ}{r} \right]_a^b$$

$$= KQ \left(\frac{1}{b} - \frac{1}{a} \right) = KQ \left(\frac{b-a}{ab} \right)$$

$$C = \frac{ab}{K(b-a)}$$

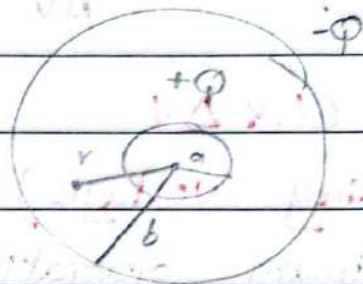

Energy stored in capacitor:

$$U = \frac{Q^2}{2C} = \frac{1}{2} Q \Delta V = \frac{1}{2} C (\Delta V)^2 \quad (\text{J})$$

← الوحدة

$$C = \frac{Q}{\Delta V}$$

* $U \propto \Delta V$, $U \propto Q$

(Breaking voltage):

maximum operating voltage of the capacitors

• Parallel plate capacitor:

$$U = \frac{1}{2} C V^2 = \frac{1}{2} \left(\frac{A \epsilon_0}{d} \right) (E d)^2 = \frac{1}{2} \underbrace{A d}_{V \rightarrow \text{volume}} \epsilon_0 E^2$$

$$\therefore U_E = \frac{1}{2} V \epsilon_0 E^2$$

$$\therefore \frac{U_E}{V} = \frac{1}{2} \epsilon_0 E^2 \Rightarrow \text{energy per volume} \\ (\text{energy density}) \quad (\text{J/m}^3)$$



ΔV

$$\text{slope} = \frac{\Delta V}{Q} = \frac{1}{C}$$

Area under the curve


= energy stored (U)

Q

• Combination in series and parallel for capacitors:

□ parallel : (القائى) الفقرة بين البطارية والمواضع

① $V_{eq} = V_1 = V_2 = V_3$

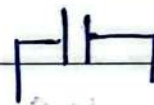


مواضع



بطارية

② $Q_{eq} = Q_1 + Q_2 + Q_3$

③ $C_{eq} = C_1 + C_2 + C_3$

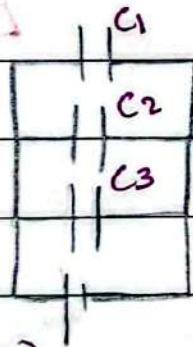

أكبر من أكبر وحدة فيهم

بطارية

2 Series : (القائى)

① $Q_{eq} = Q_1 = Q_2 = Q_3$

② $V_{eq} = V_1 + V_2 + V_3$

③ $\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \Rightarrow$

$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$


في حالة

مواضعين فقط

أقل من أقل وحدة فيهم

* Dielectric Materials:

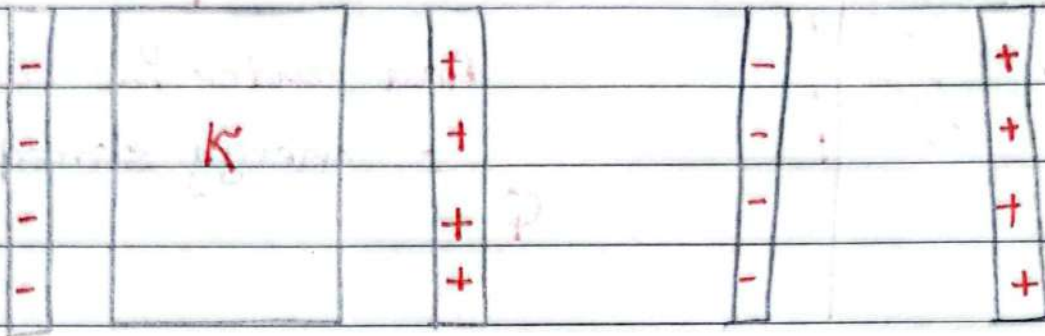→ مادة غير موصلة مثل الزجاج أو البلاستيك توضع بين الصفيحتين



$$V = \Delta V \quad \left[\begin{array}{l} \text{the same} \\ \text{after \& before} \end{array} \right] \quad V = \Delta V_0$$

$$Q = Q \quad \left[\begin{array}{l} \text{the same} \\ \text{after \& before} \end{array} \right] \quad Q_0 = Q$$

$$\Delta V = E d$$

$$= \frac{\sigma}{\epsilon} d$$

$$\epsilon = K \epsilon_0$$

$$= \frac{\sigma d}{K \epsilon_0} = \frac{\Delta V_0}{K}$$

$$\Delta V_0 = E_0 d$$

$$\Rightarrow \Delta V_0 = \left(\frac{\sigma}{\epsilon_0} \right) d$$

$$\Rightarrow C_0 = \frac{Q}{\Delta V_0}$$

K : dielectric constant

depends on the material type

$$\Rightarrow C = \frac{Q}{\Delta V} = \frac{Q K}{\Delta V_0}$$

$$\Rightarrow C = K C_0$$

before	$Q = Q$	after	
① ΔV_0		①' $\Delta V = \frac{\Delta V_0}{K}$	
② $E_0 = \frac{\Delta V_0}{d}$		②' $E = E_0 / K$	
③ $C_0 = \frac{Q_0}{\Delta V_0}$	$\Rightarrow$	③' $C = K C_0$	
④ $U_0 = \frac{Q_0^2}{2C_0}$		④' $U = \frac{U_0}{K} \rightarrow \text{decrease}$	

* minimum value for K is (1) in air
 (if $K=1$) $\Rightarrow (E = K E_0) \rightarrow (E = E_0)$

in parallel plates capacitor

$$C = K \frac{\epsilon_0 A}{d}$$

chapter (27)

Current and Resistance:

Electric current: if the flow of electric charges through a conductor (تيار كهربائي)

$$\Rightarrow I_{avg} = \frac{\Delta Q}{\Delta t}$$



↳ number of charges pass through A in unit time

مثال $I = \frac{C}{sec} = A$ (Amper)

$\Rightarrow$ instantaneous current $I = \frac{dQ}{dt}$

Microscopic model of current:

$$Q = n q_e \cdot \frac{V}{V} \quad \frac{n}{V} = n^* = \text{number of free carries per unit of Volume}$$

$$Q = n^* q_e V$$

$$\left(Q = n^* q_e (A \Delta x) \right) \div \Delta t \quad v_d = \text{drift velocity (speed)}$$

$$I = n^* q_e A v_d$$

A: cross section


$\Rightarrow [I = n^* A q_e v_d]$

$q_e = 1.6 \times 10^{-19} C$

I تيار كهربائي v_d سرعة انزياح

v_d تكون صغيرة نسبياً مقارنة بالسرعة الحقيقية للالكترونات zigzag


(11) continued

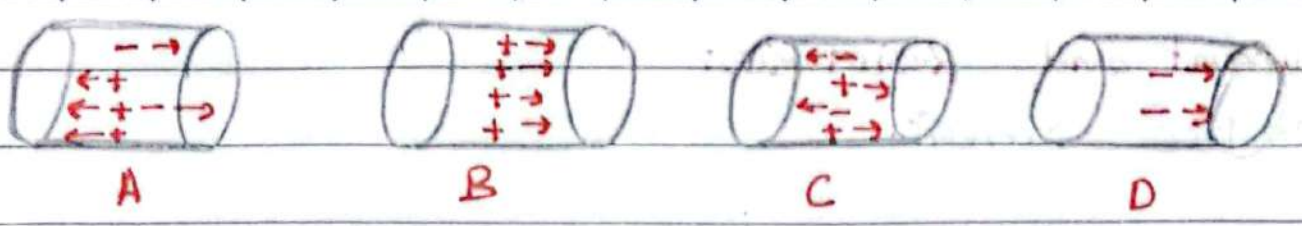

(I) (current) $\rightarrow$ $A > B \text{ and } C > D$
 الترتيب حسب عدد الشحنات الموجبة

* Current density: (J)

[non-uniform conductor]

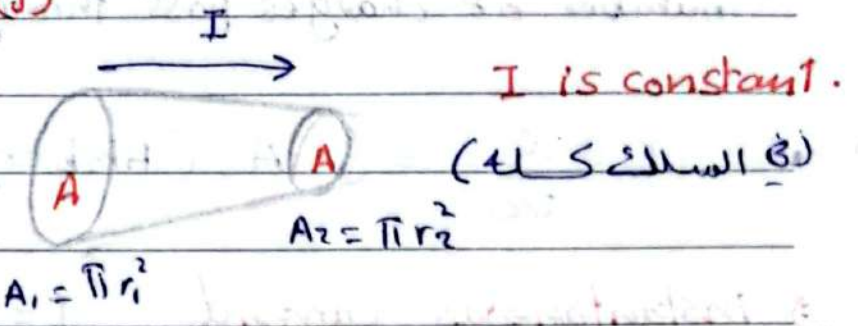

$\Rightarrow J = \frac{I}{A}$ A/m^2

$J_1 = \frac{I}{\pi r_1^2}, J_2 = \frac{I}{\pi r_2^2}$

$[I = n^+ q_e A v_d \Rightarrow J = n^+ q_e v_d]$ **

$J \propto E \rightarrow \left(\frac{I}{A} = \sigma \frac{\Delta V}{L} \right) \rightarrow \text{A/m.Volt}$

$[J = \sigma E]$

σ = electric conductivity

$\Delta V = \frac{I L}{\sigma A} = \frac{\rho L}{A} I$

$\Delta V = R I$

$\rho = \frac{1}{\sigma}$ (resistivity)

$\downarrow$
resistance

$\rightarrow \frac{m \cdot v}{A}$

$$\Delta V = \frac{R}{\Omega} \cdot I \quad \text{ohm's law}$$

$\hookrightarrow$ volt $\hookrightarrow$ Ω $\hookrightarrow$ A

$$* R = \frac{\rho L}{A} = \frac{\cancel{m} \cdot V}{A} \cdot \cancel{m} / \cancel{m^2} = \frac{V}{A} = \Omega \text{ ohm}$$

$$* \rho = \frac{RA}{L} = \frac{\Omega \cdot m^2}{m} = \Omega \cdot m$$

$$* \sigma = \frac{1}{\rho} = (\Omega \cdot m)^{-1}$$

* R depends on ρ, L, A
(Type and Shape of material)

* R independent on V and I

Power: (P) (القدرة)

* what is the power delivered in the resistor.

* what is the Heat power dissipated in the resistor

$$\left[P = I \Delta V, P = I^2 R, P = \frac{\Delta V^2}{R} \right] \Rightarrow \text{watt}$$

- Resistance and Temperature :-

ρ : depends on T & shape of material

$$\left[R(T) = R_0 (1 + \alpha \Delta T) \right] \quad \begin{matrix} \nearrow T - T_0 \\ \hookrightarrow 20^\circ C \end{matrix}$$

$\hookrightarrow$ resistance at Temp (T)

α : from Tables. (thermal Resistance coefficient) ($^\circ C^{-1}$)

R_0 resistance at $T_0 = 20^\circ C$

$$\rho = \rho_0 (1 + \alpha \Delta T) \quad \dots \quad (*)$$

$\alpha = \frac{1}{\rho_0} \frac{\rho}{\Delta T}$ (c⁻¹) [Temp. coefficient of resistivity]

I

ohmic

$$S = \frac{\Delta I}{\Delta V} = \frac{1}{R}$$

I

Non-ohmic

ΔV

ΔV

ρ

ΔV

$$S = \frac{\Delta V}{I} = R$$

$\alpha > 0$ ρ increases with T

I

T (K)



metals

ρ

increasing ↑

$\alpha < 0$

decrease with T
Semiconductors

T (K)

chapter (28)



Direct current circuits:

AC

DC

Alternating current


Direct current

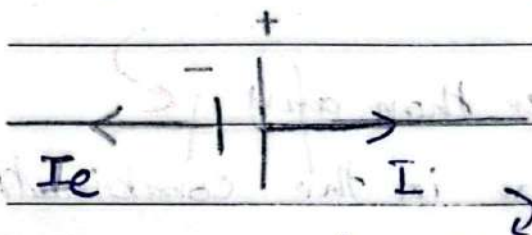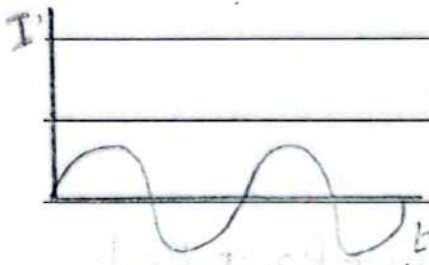

($\mathcal{E}$) $\rightarrow$ electromotive force [volt]

القوة الدافعة الكهربية

التيار الكهربائي (يتركب من عدة أجزاء)

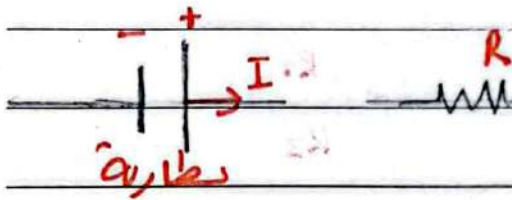

switch

wire

* Electromotive force (emf) ($\mathcal{E}$):

$$[\Delta V = \mathcal{E} - (I r)]$$

فانج عن المقاومة V_r

$$\mathcal{E} = I r + I R$$

$$P_{\text{total}} = P_r + P_R$$


$$I = \frac{\mathcal{E}}{r + R}$$

$$= I^2 r + I^2 R$$

$$\left\{ = I^2 (r + R) \right\}$$

Resistors in Series and parallel:

① Series: (سلسلة)

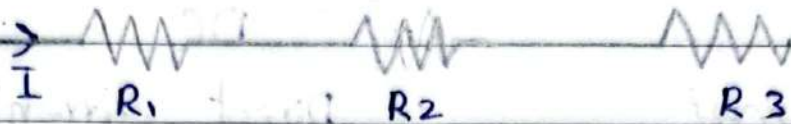

* V is divided

* current is the same in all R

$$V = V_1 + V_2 + V_3$$


$$I R_{eq} = I R_1 + I R_2 + I R_3 \Rightarrow [R_{eq} = R_1 + R_2 + R_3]$$

greater than any resistor in the combination

② Parallel

* I is divided

* V is the same in all R

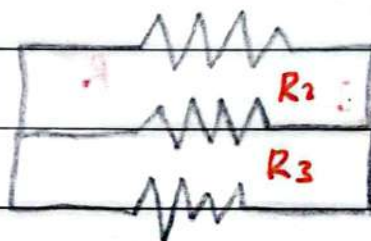

$$I_{eq} = I_1 + I_2 + I_3$$

$$\frac{V}{R_{eq}} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} \Rightarrow \left[\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right]$$

smaller than any R

$$\left[R_{eq} = \frac{R_1 \times R_2}{R_1 + R_2} \right] \text{ only Two } R$$

Chapter (25)

(مادة الفيزياء)

(25.5) Electric potential due to continuous charge distribution:


$$\rho = \frac{Q}{V}, \quad \sigma = \frac{Q}{A}, \quad \lambda = \frac{Q}{L}$$

$$dV = k_e \frac{dq}{r}$$

$$V_P = k_e \int \frac{dq}{r}$$

rod

1

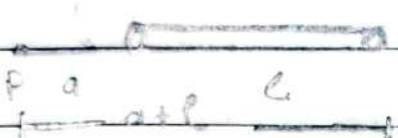


$$V = k\lambda \ln\left(\frac{a+L}{a}\right)$$

constant (\$\lambda\$)


$$[V_P = k\lambda L] \rightarrow \lambda \text{ not cont.}$$

2 ring

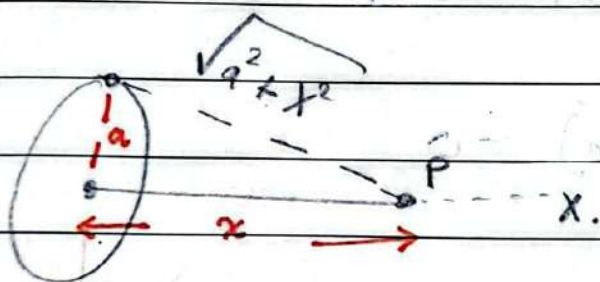

$$V = \frac{k_e Q}{\sqrt{x^2 + a^2}}$$

3 arc

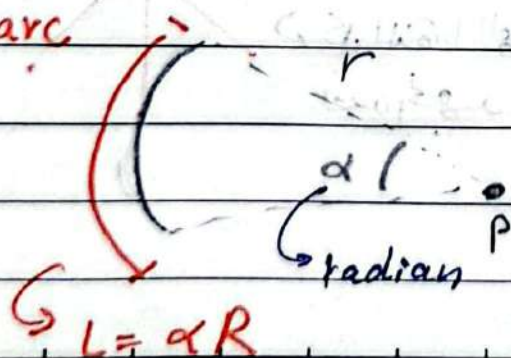


$$V = k_e \lambda \alpha$$

(or)

$$V = k \frac{Q}{R} \quad \text{where } Q = \lambda \alpha R$$

[4] rod (قضبان)

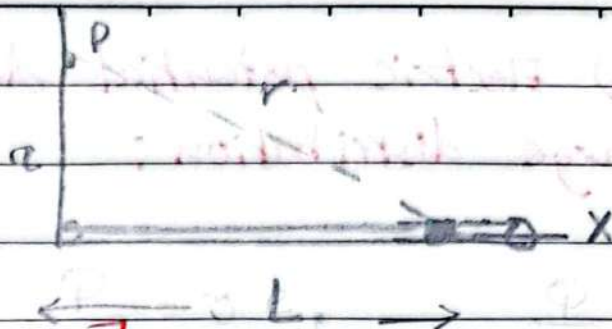

$$V = k_e \lambda \left(\frac{1 + \sqrt{a^2 + L^2}}{a^2} \right)$$


(25.6) Equipotential surfaces:

↳ surfaces with the same (V)

$$\Delta V = -E d \cos \theta$$

$$V_{ab} = V_b - V_a = -E d \cos 90$$
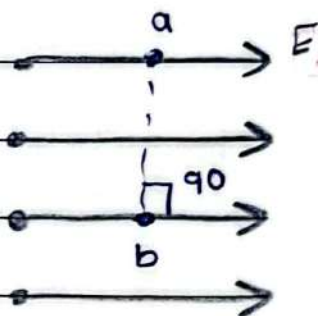
$$V_b - V_a = 0 \Rightarrow [V_b = V_a]$$



خطوط التساوي (النقطة) بزاوية 90 مع $\underline{E}$

$$U_{a \rightarrow b} = q (V_b - V_a) = 0$$

(مفرد).

$$V = k \frac{q}{r}$$

$$U_{a \rightarrow b} = 0$$

$$W_{a \rightarrow b} = 0$$

كل النقاط لها نفس الجهد

