



اللجنة الأكاديمية للهندسة المدنية

دفتر

الفيزياء العامة 2

راما السعدي

Contact us:

f Civilittee HU | لجنة المدني

▶ Civilittee Hashemite


www.civilittee-hu.com



Ch. 26

* Capacitance and dielectric

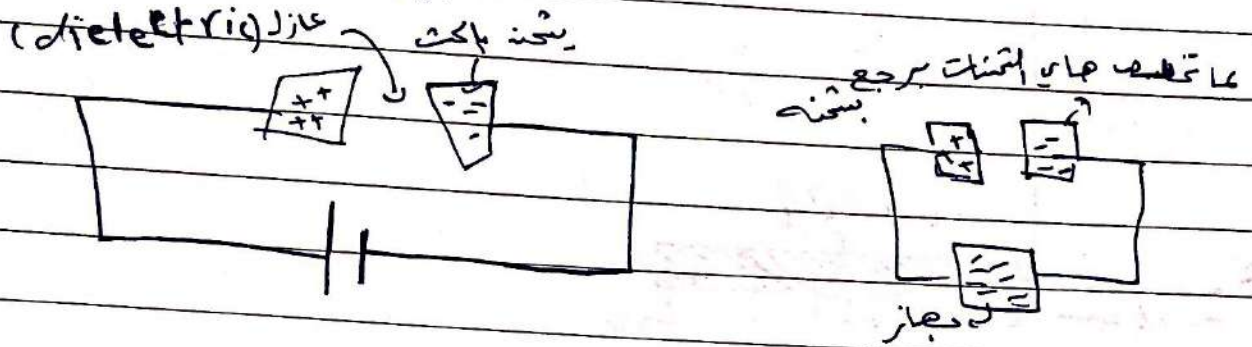Capacitance is a device that store electrical charges (electrical energy)



$$Q \propto V \Rightarrow Q = C \cdot V$$

$$Q = C \cdot V \quad C: \text{Capacitance}$$


$$C = \frac{Q}{V}$$

علاقة بين الشحنة والجهد
 $V \rightarrow Q$

C = ratio between Q and V

* C depends only on the geometry of the capacitor.

i.e.

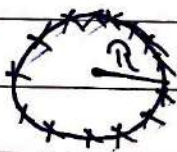


$$C = \frac{q}{V}, \quad V = \frac{kq}{R} \Rightarrow C = \frac{qR}{kq}$$

$$C = 4\pi\epsilon \cdot R$$

let the earth to be the capacitor $R = 6400 \text{ km}$

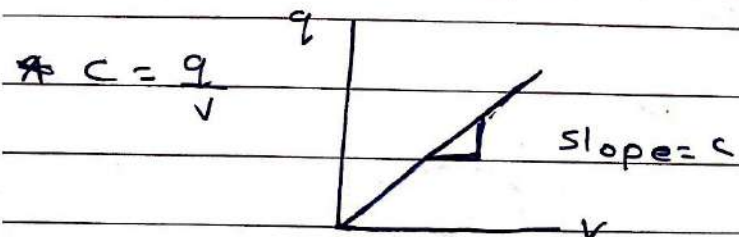
$$C_{\text{earth}} \approx 7 \times 10^{-4} \text{ f} < 1 \text{ mf}$$





* Calculating the capacitance.

① parallel plate capacitor

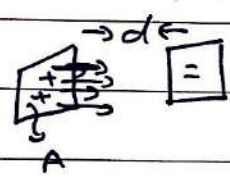

From G.L :-

the electric field for a plate $E = \frac{\sigma}{2\epsilon_0}$


for parallel plate capacitor

$$E = E_1 + E_2 = \frac{\sigma}{\epsilon_0}$$

$$\text{and } V = Ed = \frac{\sigma}{\epsilon_0} d = \frac{q d}{A \epsilon_0}$$

$$\Rightarrow C_p = \frac{q}{V} = \frac{q A \epsilon_0}{q d} \Rightarrow \boxed{C_p = \frac{\epsilon_0 A}{d}} \quad C_p \propto \frac{A}{d}$$

2] Cylindrical capacitor

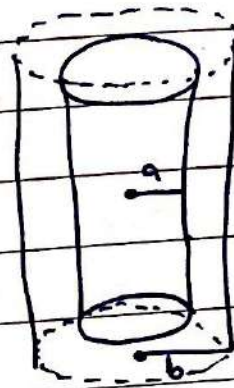

$$V_b - V_a = - \int \vec{E} \cdot d\vec{r}$$

but $E = \frac{2ke\lambda}{r}$

$$\Delta V = -2ke\lambda \int_a^b \frac{dr}{r}$$


$$= -2ke\lambda \ln r \Big|_a^b$$

$$\Delta V = -2ke\lambda \ln(b/a)$$

$$|C| = \frac{q}{\Delta V} = \frac{2L}{2ke\lambda \ln(b/a)} \Rightarrow C_{cy} = \frac{L}{ke \ln(b/a)}$$


H.W. 3] Spherical capacitor.

$$C = \frac{ab}{ke(b-a)}$$

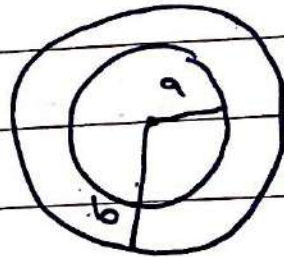

* Combination of capacitors :-

1) series connection

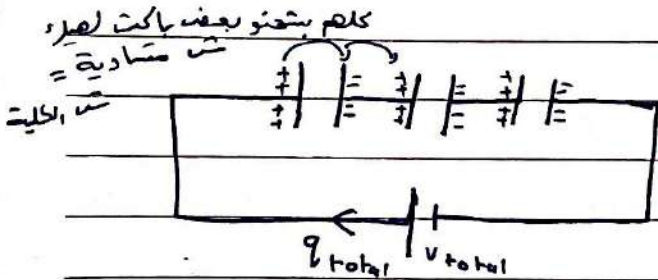

$$q_{total} = q_1 = q_2 = q_3$$


$$V_{total} = V_1 + V_2 + V_3 \quad \text{but} \quad V = \frac{q}{C}$$

$$\frac{q_{total}}{C_{total}} = \frac{q_1}{C_1} + \frac{q_2}{C_2} + \frac{q_3}{C_3}$$

متسارئة
مت الكلية

$$\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

2) parallel connection

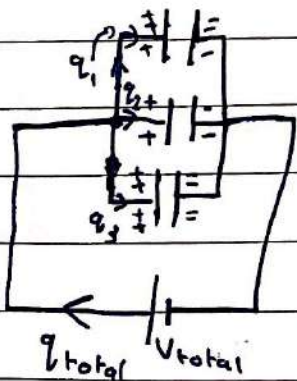

$$q_{total} = q_1 + q_2 + q_3$$

$$V_{total} = V_1 = V_2 = V_3$$


$$\text{but } q = CV$$

$$C_{total} \times V_{total} = C_1 V_1 + C_2 V_2 + C_3 V_3$$

$$C_p = C_1 + C_2 + C_3$$



Energy stored in capacitor

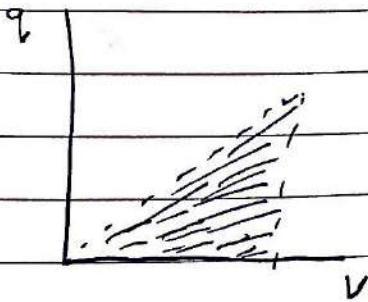

$$U = \frac{1}{2} \frac{q^2}{C}$$

$$W = qV$$

$$dW = q dV$$

$$\int dW = \int CV dV$$

$$W = \frac{1}{2} CV^2$$

Energy = Area

$$U = \frac{1}{2} qV$$

$$q = CV$$

$$U = \frac{1}{2} CV^2$$

For parallel plate capacitor

$$C = \frac{\epsilon_0 A}{d}$$

$$V = Ed$$

$$U = \frac{1}{2} CV^2 = \frac{1}{2} \frac{\epsilon_0 A}{d} E \cdot d^2$$

$$U = \frac{1}{2} \epsilon_0 A E^2 d$$

$$= \frac{1}{2} \underbrace{Ad}_{\text{Volume}} \epsilon_0 E^2$$

⇒ Define energy density u

$$u = \frac{U}{Ad} \Rightarrow \boxed{u = \frac{1}{2} \epsilon_0 E^2} \text{ energy density}$$



* capacitor with dielectric

ثابت العزل

dielectric constant $K > 1$

$$\epsilon_0$$

ثابت العزل

$$* \epsilon_{\text{vacuum}} = 1$$


dielectric increases the capacitors

$$C_0 \Rightarrow C = K C_0 \rightarrow \text{ما الكم دخلنا ونضالته}$$


$$\text{Ex } C_0 = \frac{\epsilon_0 A}{d} \text{ (air)}$$

$$C = K C_0 = (K \epsilon_0) \frac{A}{d}$$
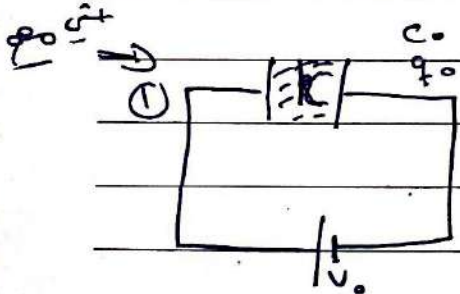
$$\epsilon = K \epsilon_0 \Rightarrow \epsilon > \epsilon_0$$



(2)

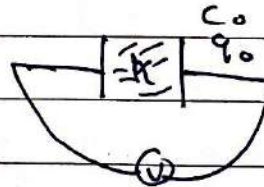

$$C = K C_0$$

$$q = K q_0$$

$$V = \frac{q}{C} = \frac{K q_0}{K C_0}$$

$$V = V_0$$

$$C = K C_0$$

$$q = q_0$$


$$V = \frac{q}{C}$$

$$V_0 = \frac{q_0}{K C_0}$$

$$V = \frac{V_0}{K}$$




③

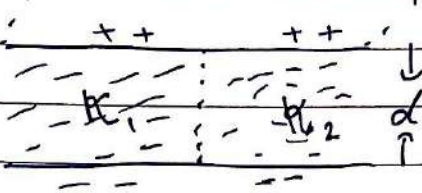

* ما يكون بالتف

فأنة حسب الحالة

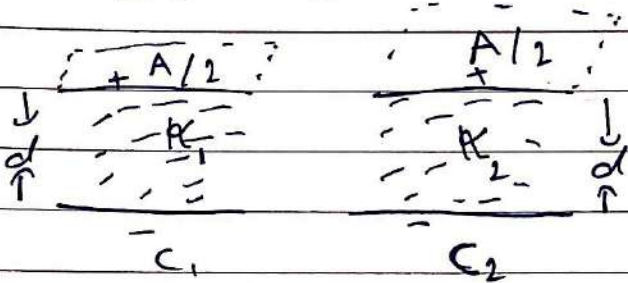




$$C_1 = \frac{K_1 \epsilon_0 A/2}{d}$$

$$C_2 = \frac{K_2 \epsilon_0 A/2}{d}$$

$C_{total} \Rightarrow C_1$ and C_2 in parallel

$$C_{total} = C_1 + C_2$$

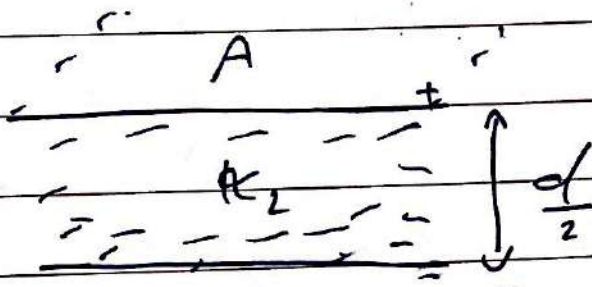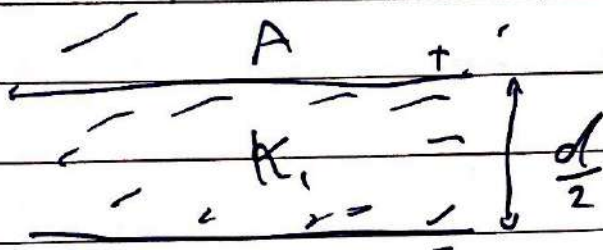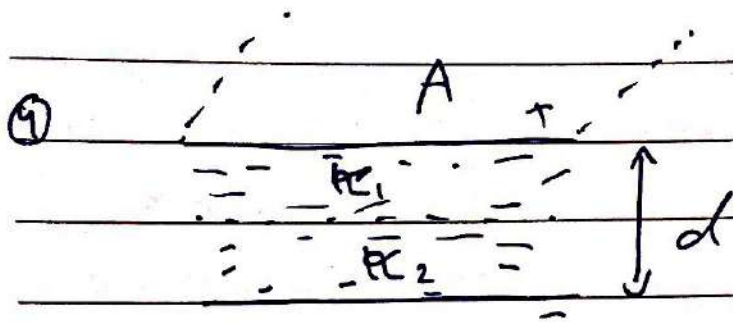
$$= \frac{K_1 \epsilon_0 A}{2d} + \frac{K_2 \epsilon_0 A}{2d} = \frac{\epsilon_0 A}{2d} (K_1 + K_2)$$





$$C_1 = \frac{2 \kappa_1 \epsilon_0 A}{d}, \quad C_2 = \frac{2 \kappa_2 \epsilon_0 A}{d}$$

$C_{\text{total}} \Rightarrow C_1$ and C_2 in series
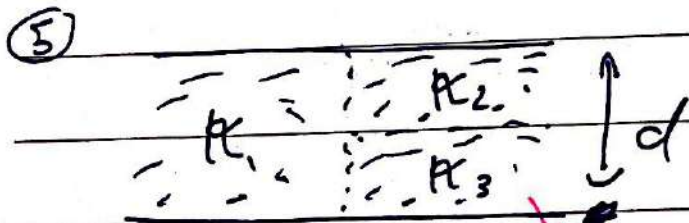
$$\frac{1}{C_{\text{total}}} = \frac{1}{C_1} + \frac{1}{C_2}$$



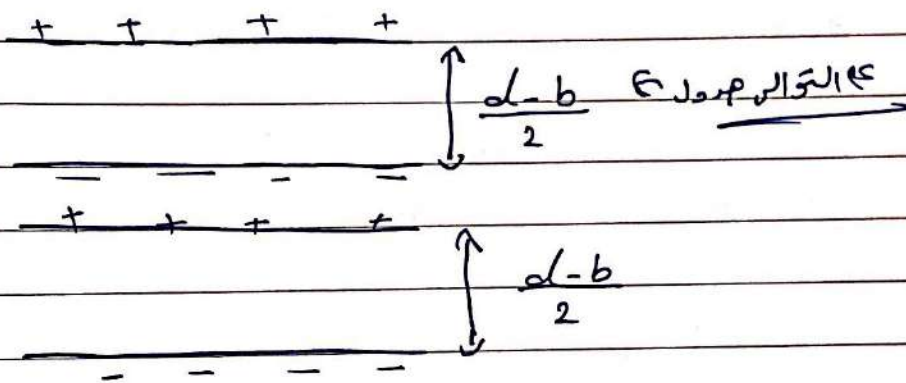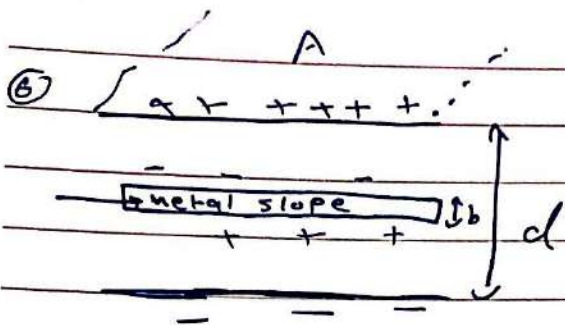→ $\kappa_1, \kappa_2, \kappa_3$ are in series




* dielectric strengths-

max electric field that can be applied to the dielectric before breaking

	ϵ_r	$E_{max} \times 10^6$
Air	1.00059	3
Teflon	2.1	60
paraelian	6	12



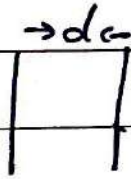7 $V = 150 \text{ V}$ $\sigma = 30 \text{ nc/cm}^2$ $d = ??$



$$V = \frac{q}{C} = \frac{\sigma A d}{\epsilon \cdot A} = \frac{\sigma d}{\epsilon}$$

بالتالي $\epsilon = 8.85 \times 10^{-12}$

$$150 = \frac{30 \times 10^{-9} \times 10^{-4}}{8.85 \times 10^{-12}} \times d \Rightarrow d = 9.4 \text{ mm}$$

9 $A = 7.6 \text{ cm}^2$ $d = 1.8 \text{ mm}$ $V = 20 \text{ V}$

a) $E = \frac{V}{d} = \frac{20}{1.8 \times 10^{-3}} = 1.1 \times 10^4$


b) $E = \frac{\sigma}{\epsilon} \Rightarrow \sigma = 1.1 \times 10^4 \times 8.85 \times 10^{-12}$
 $\sigma = 9.8 \times 10^{-8} \text{ C/m}^2$

c) $C = \frac{\epsilon \cdot A}{d} = 3.7 \text{ pf} \Rightarrow 10^{-12}$

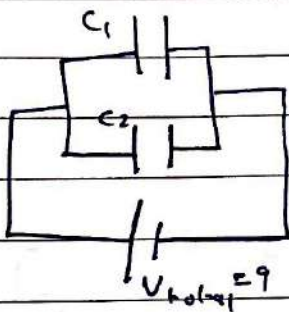d) $q = \sigma A = CV$

$$9.8 \times 10^{-8} \times 7.6 \times 10^{-4} = 7.5 \times 10^{-11}$$

13 $C_1 = 5 \text{ MF}$ $C_2 = 12 \text{ MF}$ $V = 9 \text{ V}$




a) $C_p = C_1 + C_2 = 17 \text{ MF}$

b) $V_1 = V_2 = 9 \text{ V}$

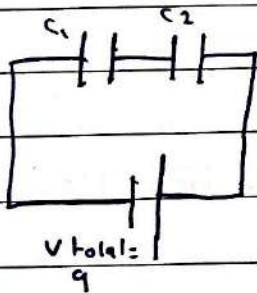c) $q_1 = C_1 V_1$
 $= 5 * 9 = 45 \text{ MC}$

$q_2 = C_2 V_2 = 12 * 9 = 108 \text{ MC}$

14 $C_1 = 5 \text{ MF}$ $C_2 = 12 \text{ MF}$ $V = 9 \text{ V}$




a) $\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{5} + \frac{1}{12} = 3.5 \text{ MF}$

b) $q_1 = q_2 = q_{\text{total}} = C_s * V_{\text{total}}$
 $= 9 * 3.5 = 31.5 \text{ MC}$

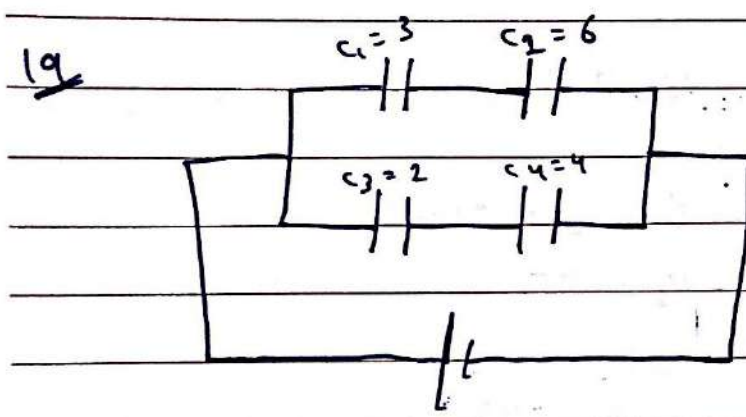
c) $V_1 = \frac{q_1}{C_1} = \frac{31.5}{5} = 6.3 \text{ V}$

$V_2 = 9 - 6.3 = 2.7 \text{ V}$
 $V_2 = \frac{q_2}{C_2} = \frac{31.5}{12} = 2.7 \text{ V}$



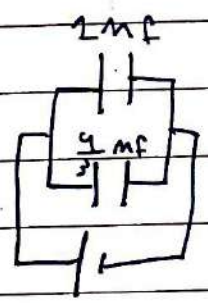a) $(C_1, C_2) \rightarrow s \Rightarrow \frac{1}{C_{S1}} = \frac{1}{C_1} + \frac{1}{C_2} \Rightarrow \boxed{C_{S1} = 2 \text{ MF}}$

$(C_3, C_4) \rightarrow s \Rightarrow \frac{1}{C_{S2}} = \frac{1}{C_3} + \frac{1}{C_4} \Rightarrow \boxed{C_{S2} = \frac{4}{3} \text{ MF}}$





$(C_{S1}, C_{S2}) \rightarrow p \Rightarrow C = \frac{10}{3} \text{ MF}$

b) $q_1 = q_2 = q_{C_{S1}} = V_{C_{S1}} = 90 \times 2 \Rightarrow q_1 = q_2 = 180 \text{ mC}$


$q_3 = q_4 = q_{C_{S2}} = V_{C_{S2}} = 90 \times \frac{4}{3} \Rightarrow q_3 = q_4 = 120 \text{ mC}$

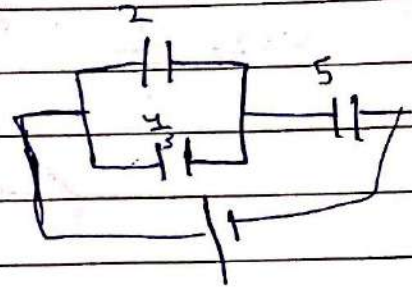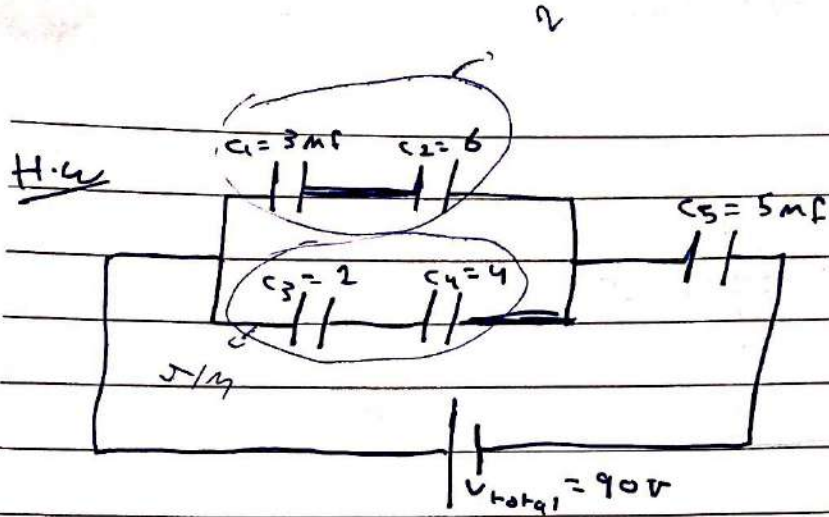c) $V_1 = \frac{q_1}{C_1} = \frac{180}{3} = 60 \text{ V}$ so $V_2 = 90 - 60 = 30 \text{ V}$

$V_3 = \frac{q_3}{C_3} = \frac{120}{2} = 60 \text{ V}$ so $V_4 = 90 - 60 = 30 \text{ V}$


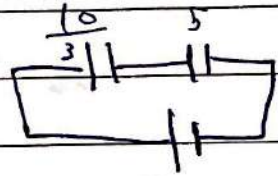
$$C_s = \frac{1}{\frac{1}{3} + \frac{1}{6}} + \frac{1}{\frac{1}{2} + \frac{1}{4}} = \frac{5}{10} = \frac{10}{5} = 2$$



$$q = 90 \times 2 = 180$$

$$C_5 \Rightarrow q = 180 \Rightarrow V = \frac{180}{5} = 36$$

$$C_{\left(\frac{10}{3}\right)} \Rightarrow V = 90 - 36 = 54\text{V} \Rightarrow q = 180\text{mC}$$

$$C_{(2)} \Rightarrow V = 54 \Rightarrow q = 54 \times 2 = 108\text{mC}$$

$$C_{\left(\frac{4}{3}\right)} \Rightarrow V = 54 \Rightarrow q = 54 \times \frac{4}{3} = 72\text{mC}$$

$$C_1 \Rightarrow q = 108 \Rightarrow V = \frac{108}{3} = 36$$


$$C_2 \Rightarrow q = 108 \Rightarrow V = \frac{108}{6} = 18$$

$$C_3 \Rightarrow q = 72 \Rightarrow V = \frac{72}{2} = 36$$

$$C_4 \Rightarrow q = 72 \Rightarrow V = \frac{72}{4} = 18$$




24

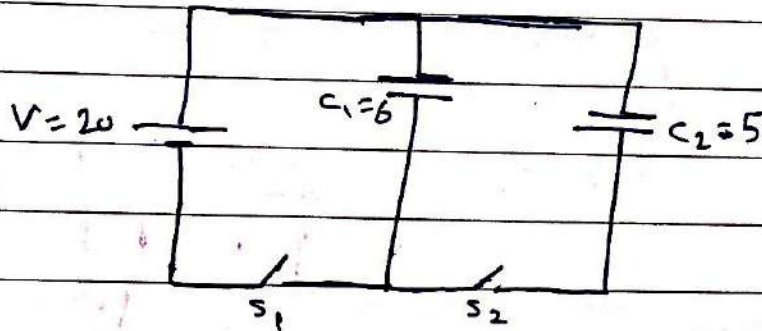

S_1 close ~~✓~~ S_2 open

$$q_1 = C_1 V = 120 \text{ } \mu\text{C}$$

S_1 open S_2 close

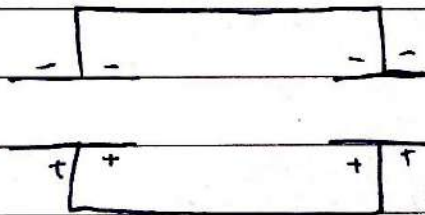

$$V_1 = V_2$$

$$\frac{q_1}{C_1} = \frac{q_2}{C_2} \Rightarrow \frac{q_1}{6} = \frac{q_2}{5}$$

$$2q_2 = q_1$$

but $\sum q_i = \sum q_f$

$$120 + 0 = q_1 + q_2$$

$$120 = 3q_2 \Rightarrow q_2 = 40 \text{ } \mu\text{C}$$

$$q_1 = 120 - 40 = 80 \text{ } \mu\text{C}$$

$$V_1 = \frac{q_1}{C_1} = \frac{80}{6} = \frac{40}{3} \text{ } \mu\text{V}$$

$$V_2 = \frac{q_2}{C_2} = \frac{40}{5} \text{ } \mu\text{V}$$


43 $A = 5 \text{ cm}^2$ $E_{\text{max}} = 3 \times 10^6 \text{ V/m}$

$q_{\text{max}} = ?$

$E_{\text{max}} = \frac{\sigma_{\text{max}}}{\epsilon_0} = \frac{q_{\text{max}}}{\epsilon_0 \cdot A}$

$q_{\text{max}} = E_{\text{max}} \cdot \epsilon_0 \cdot A = 13.3 \text{ nC}$

44

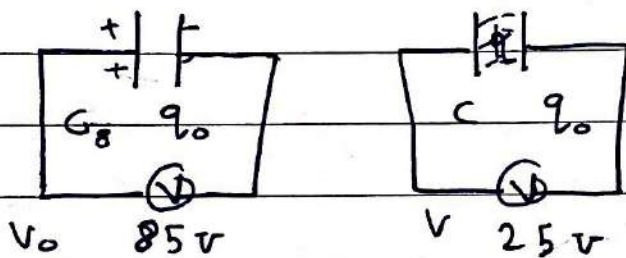

$R = ?$

$V_0 = \frac{q_0}{C_0}$ $V = \frac{q_0}{R} = \frac{q_0}{R C_0} V_0$

$V = \frac{V_0}{R} \Rightarrow R = \frac{85}{25} = 3.4$

Ch. 27.

Current and Resistance.

Current is flow of charges between two points due to a potential difference.

$I \equiv$ charge per unit of

$$I = \frac{\Delta q}{\Delta t}$$




$$\frac{2 \Delta}{\Delta} = C$$

$$I = \frac{dq}{dt} \Rightarrow \int_{q_i}^{q_f} dq = \int_a^t I \cdot dt$$


$$\Delta q = \int_0^t I \cdot dt$$

if I constant $\Rightarrow \Delta q = I \Delta t$

Current direction

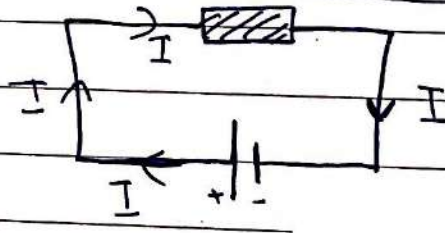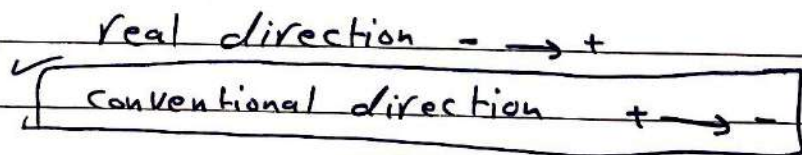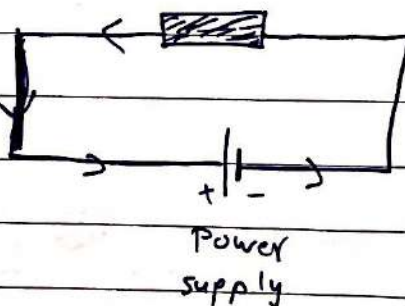

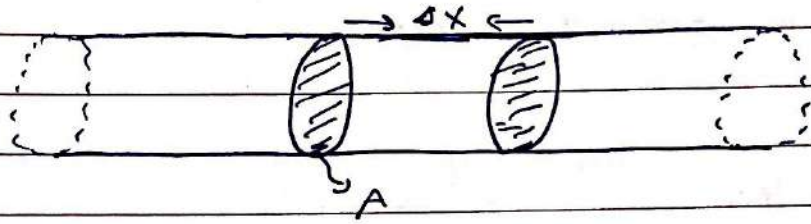The charges flow from high potential to low potential



n free charge density \Rightarrow number of free charges per unit volume.

\Rightarrow number of charge = $n \times \text{Volume} = n \times A \Delta x$

but $\Delta x = v \Delta t$

\Rightarrow number of charges = $n A v \Delta t$

charge = number of charge $\times e$

$$\frac{q}{\Delta t} = \frac{n A v \Delta t e}{\Delta t}$$

$$I = n A v e$$


$$e \vec{v} = \vec{E} \Rightarrow \vec{v} = \frac{\vec{E}}{E} v$$

$n \equiv$ Charge density electron/ m^3

$A \equiv$ cross-section area m^2

$e \equiv 1.6 \times 10^{-19} \text{ C}$

$v_d \equiv$ drift velocity m/s

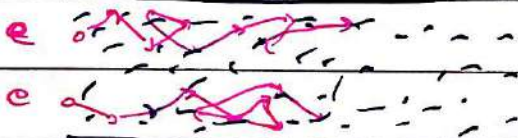

\Rightarrow electrical Resistance R and
ohm's law



* Define :- the current density \vec{J}

$$\vec{J} = \frac{I}{A} \text{ current per unit of Area}$$

* Ohm's law


\vec{J} and \vec{E} relation

He founds that

$$\vec{J} \propto \vec{E} \Rightarrow \vec{J} = \sigma \vec{E} \quad \text{Ohm's law}$$

σ - is the conductivity of the

$$E = \frac{V}{L}$$

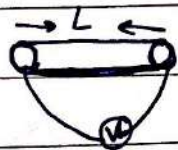

$$\therefore \frac{I}{A} = \frac{\sigma V}{L}$$

$$J = \frac{I}{A}$$

$$\Rightarrow V = \frac{L I}{\sigma A}$$

$$V = \frac{L I}{\sigma A}$$

$$V = \frac{\rho L I}{A}$$

ρ resistivity
 $\frac{\rho L}{A}$
Resistance R

$$V = I R$$

where $R = \frac{\rho L}{A}$

$$I = \frac{\Delta q}{\Delta t} ; \vec{J} = \frac{dq}{dt}$$

$$I = n \vec{v} A e$$


$$\vec{J} = \sigma \vec{E}$$

$$V = IR$$


$$R = \frac{\rho L}{A}, R = \frac{V}{I} \text{ const (I, V & } \rho \text{ are const)}$$

$$\rho = \frac{1}{\sigma}$$

$$\rho = \frac{RA}{L}$$

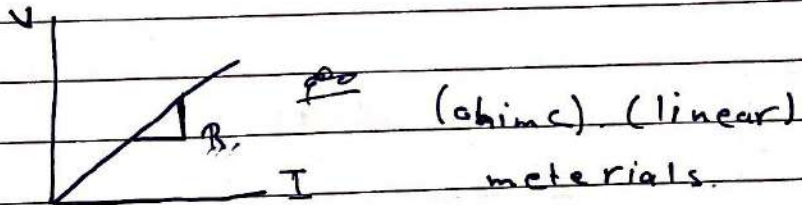

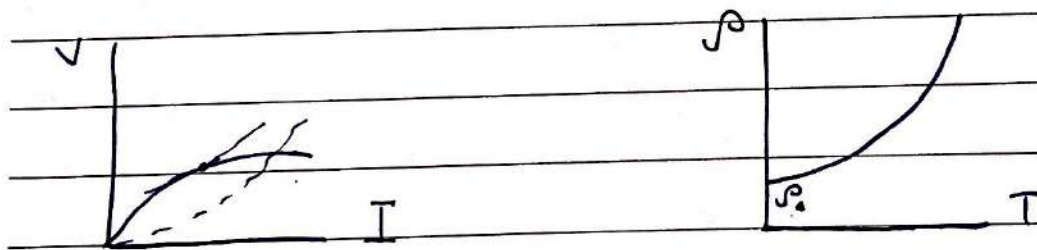* ρ depends only on material type and temp



non-ohmic materials

* Resistance and temperature:

$$\rho = \rho_0 [1 + \alpha \Delta T]$$

ρ_0 : resistivity at known temperature

ΔT : temperature difference $T_f - T_i$

α : temperature coefficient of Resistivity.

$$R = R_0 [1 + \alpha \Delta T]$$



* Electric power

القوة

$P \equiv$ work (energy) done per unit of time.

$$P = \frac{U}{t}$$

$$P = \frac{dU}{dt} = \frac{d(qV)}{dt}$$

$$P = V \frac{dq}{dt} \Rightarrow P = IV$$

oR:

$$P = \frac{\vec{F} \cdot d\vec{l}}{t} = \left(\frac{q}{t} \right) (\vec{E} \cdot d\vec{l})$$

$$P = IV = I^2 R = \frac{V^2}{R} \Rightarrow V = Pt$$

$$[V] = w.s$$

$$= kw.h$$

$$I = I_0 e^{-t/\tau}$$

$$q = t \cdot I = 0 \rightarrow t = \tau$$

$$I = \frac{dq}{dt} \Rightarrow dq = I dt$$

$$\int dq = \int I dt$$

$$q = \int_0^{\tau} I_0 e^{-t/\tau} dt$$

$$= -\tau I_0 \left[e^{-t/\tau} \right]_0^{\tau}$$

$$= -\tau I_0 [e^{-1} - 1]$$

$$q = 0.63 I_0 \tau$$

b, c H.W

16 $V = 0.9 \text{ V}$ $l = 1.5 \text{ m}$ $A = 0.6 \text{ mm}^2$ $I = ?$

$V = IR$; $R = \frac{\rho l}{A} = \frac{\rho * 1.5}{0.6 \times 10^{-6}}$ from table.

P 18 $l_{Al} = l_{Cu}$, $R_{Al} = R_{Cu}$

$\frac{V_{Al}}{r_{Cu}} = ?$

$\Rightarrow R_{Al} = R_{Cu}$

$\frac{\rho_{Al} l_{Al}}{\pi r_{Al}^2} = \frac{\rho_{Cu} l_{Cu}}{\pi r_{Cu}^2}$

$\frac{r_{Al}}{r_{Cu}} = \sqrt{\frac{\rho_{Al}}{\rho_{Cu}}}$

26 $T = 20 \text{ }^\circ\text{C}$ $R_0 = 19 \text{ } \Omega$ $\Rightarrow T = \text{hot}$ $R = 140$, $(T_f = ?)$ $\alpha = 4.5 \times 10^{-3}$
from table

$R = R_0 [1 + \alpha \Delta T]$ $\Delta T = T_f - T_i$

$140 = 19 [1 + 4.5 \times 10^{-3} \Delta T]$

$\Delta T = 1415 \text{ }^\circ\text{C} \Rightarrow T_f = 1415 + 20$

$T_f = 1435 \text{ }^\circ\text{C}$

33 $r = 0.05 \text{ mm}$ $E = 0.2 \text{ V/m}$ $T = 50^\circ \text{C}$ $l = 2 \text{ m}$

a) ~~$R = \frac{\rho l}{A}$~~ $R = \frac{\rho l}{A} = \frac{2.8 \times 10^{-8} \times 2}{\pi (0.05 \times 10^{-3})^2} = 7.13 \Omega$

b) $J = \sigma E$

$$= \frac{1}{\rho} E = \frac{0.2}{2.8 \times 10^{-8}} \Rightarrow J = 7.14 \times 10^6 \text{ A/m}^2$$

c) $J = \frac{I}{A} \Rightarrow I = JA = 7.14 \times 10^6 \times \pi (0.05 \times 10^{-3})^2$

$$I = 0.06 \text{ A}$$

d) $n = 6 \times 10^{28} \text{ electron/m}^3$

$$I = n v A e$$

$$0.06 = 6 \times 10^{28} \times v \times (\pi (0.05 \times 10^{-3})^2) \times 1.6 \times 10^{-19}$$

$$v = 8 \times 10^{-4} \text{ m/s} = 0.8 \text{ mm/s}$$

e) $v = I r = E \cdot d$

$$0.06 \times 7.13 = 0.43 \text{ V}$$

35 at what T $\Rightarrow \rho_{Al} = 3 \rho_{Cu}$

$\rho_{Al} = 3 \times 1.7 \times 10^{-8}$

$\rho = \rho_0 [1 + \alpha \Delta T]$

$3.17 \times 10^{-8} = 2.8 \times 10^{-8} [1 + 3.9 \times 10^{-3} \Delta T]$ $T_f = 20$

$T_f = ?$

47 $I = 1.7 A$ $V = 110 v$

$P = \frac{U}{t} \Rightarrow U = P t = I V t$

$P = 1.7 \times 110 \times 24 \times 3600 = 1.62 \times 10^7 J$

مقدار العمل المبذور
مصدر واط / س
بدي كيلو واط / ساعة


$P = \frac{1.7 \times 110}{1000} \times 24 = 4.5 \text{ kW.h}$

cost = $4.5 \times 0.11 \$ = 0.5 \$$

ch. 28


Direct current circuits

Electromotive force.

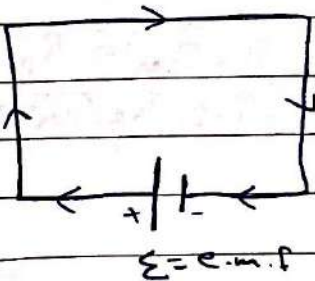

e.m.f = work needed to move charge

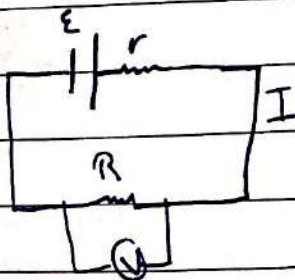from - to + or from + to -
inside the battery at side




$$\epsilon = V_r + V_R$$

$$\epsilon = Ir + IR$$

$$\Rightarrow V_R = \epsilon - (Ir) \text{ Voltage}$$

$$V_R = \epsilon - (Ir) \text{ drop}$$

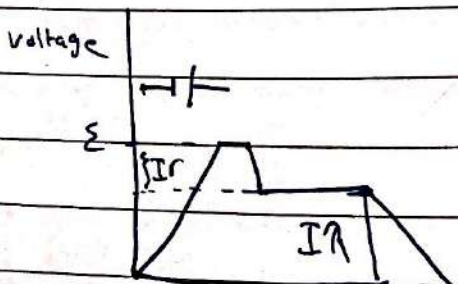

So $\epsilon = I(r + R)$


$$I = \frac{\epsilon}{r + R}$$

components In general

$$I = \frac{\epsilon}{\epsilon r + \epsilon R}$$

$$\frac{\epsilon}{r + R} = I$$



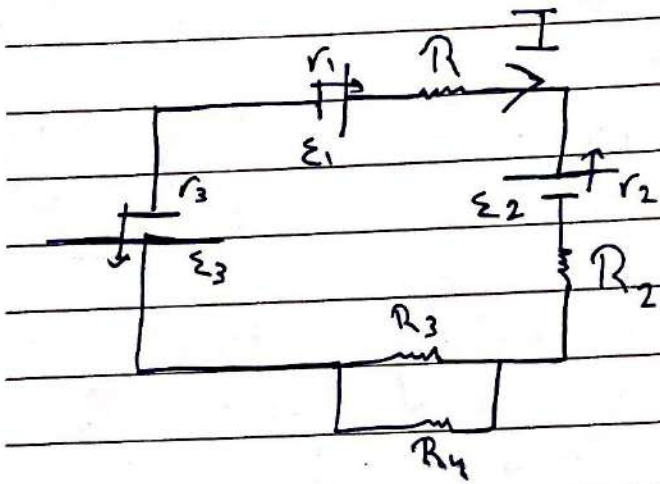

$$I = \frac{\epsilon_1 - \epsilon_2 - \epsilon_3}{(r_1 + r_2 + r_3) + \Sigma R}$$

$$R_2, R_3 \Rightarrow R_p$$

$$R_p, R_2, R_3 \Rightarrow R_s$$

$$\ast (\epsilon = Ir + IR) \ast I$$

$$\underbrace{I\epsilon}_{\text{Power}} = \underbrace{I^2 r}_{\text{dissipated}} + \underbrace{I^2 R}_{\text{Power}}$$

$$\ast (\epsilon = V_r + V_R) \ast q$$

$$\Sigma q = \underbrace{q V_r}_{\text{work}} + \underbrace{q V_R}_{\text{work}}$$

* Resistance connection

$$R_p \Rightarrow R_1 + R_2 + R_3 + \dots$$

~~$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$~~


* Kirchoff's Rules :-

Rule 1:-

$$\sum I_{in} = \sum I_{out} \text{ of node}$$

$$\sum I_{in} - \sum I_{out} = 0$$

$$\sum I = 0 \text{ at node}$$

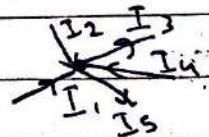

$$I_1 + I_2 + I_4 = I_3 + I_5$$


$$I_1 + I_2 + I_4 - I_3 - I_5 = 0 \text{ at node}$$

Conservation of charge

Rule 2:-

$$\sum V = 0 \text{ closed track}$$

\Rightarrow conservation of energy

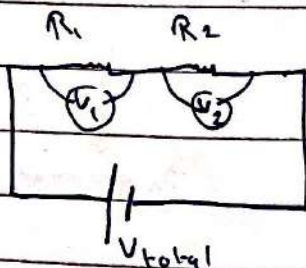


$$V_{total} = V_1 + V_2$$

$$V_{total} - V_1 - V_2 = 0$$

$$\sum \Delta V = 0$$



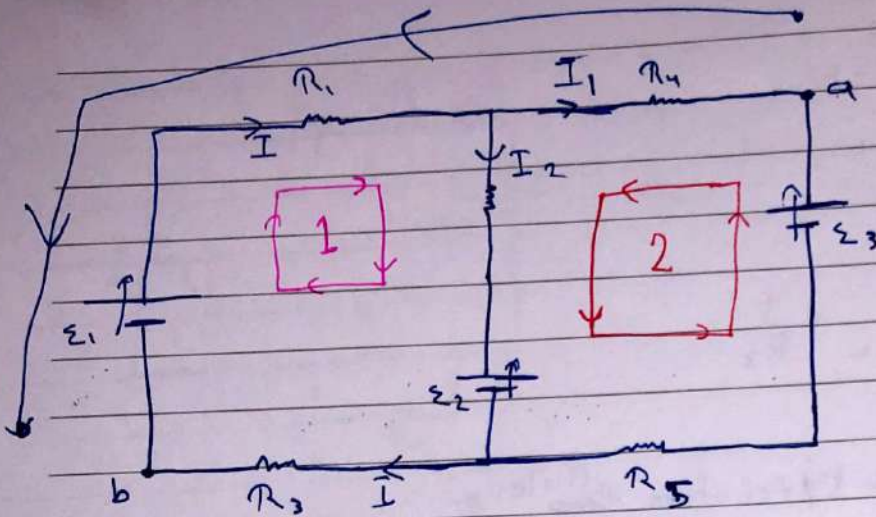

$$I = I_1 + I_2$$

loop 1:-


$$-IR - I_2 R_2 - \epsilon_2 - IR_3 + \epsilon_1 = 0$$

loop 2:-

$$I_1 R_4 - I_2 R_2 - \epsilon_2 + I_1 R_5 + \epsilon_3 = 0$$


$$V_{ab} = V_a - V_b$$
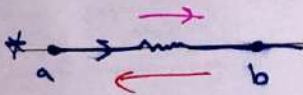
$$V_a + I_1 R_4 + I_1 R_1 - \epsilon_1 = V_b$$




$$V_a > V_b \Rightarrow \Delta V = V_b - V_a < 0$$
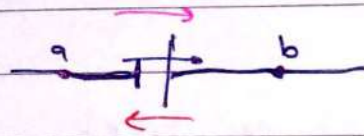
$$V_a < V_b \Rightarrow \Delta V = V_b - V_a > 0$$



$$V_a < V_b \Rightarrow \Delta V = V_b - V_a > 0$$
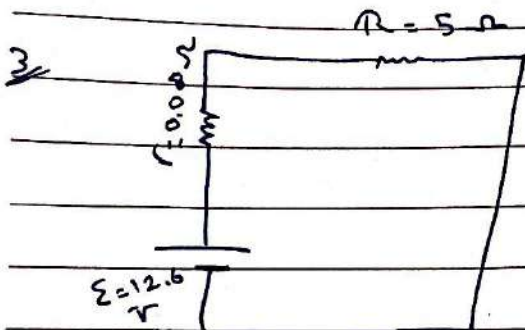
$$V_a > V_b \Rightarrow \Delta V = V_a - V_b < 0$$




$$V_R = \varepsilon - V_r \quad \text{but} \quad I = \frac{\varepsilon}{R+r} = \frac{12.6}{5+0.08} = 2.48 \text{ A}$$

$$V_R = \varepsilon - I r$$

$$= 12.6 - 2.48 * 0.08$$

$$= 12.4 \text{ V}$$

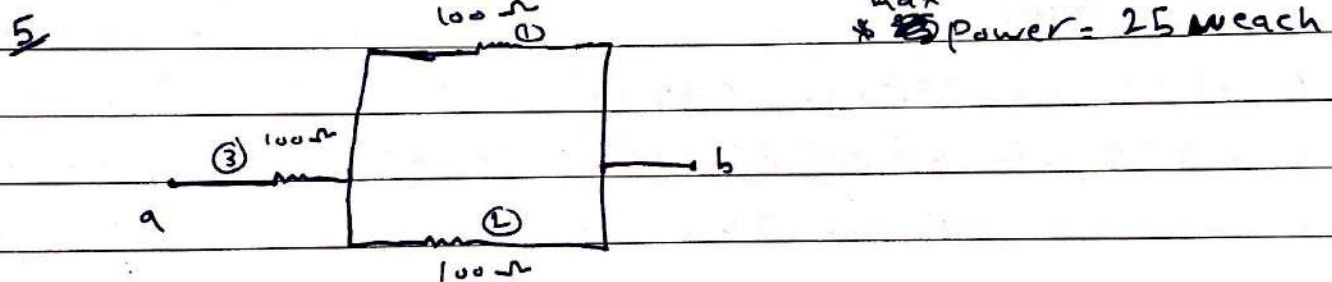

$$\textcircled{1} \quad P_1 = I_1^2 R_1 \Rightarrow 25 = I^2 * 100$$

$$\Rightarrow I_1 = 0.5 \text{ A} = I_2$$


$$\downarrow$$

$$V_1 = I_1 R_1 = 0.5 * 100 = 50 \text{ V}$$

$$I_3 = I_1 + I_2 = 0.5 + 0.5 = 1 \text{ A}$$

$$P_3 = 25 \text{ W} = I_3 V_3 \Rightarrow 25 = 1 * V_3 \Rightarrow V_3 = 25 \text{ V}$$

$$V_{ab} = 25 + 50 = 75 \text{ V}$$

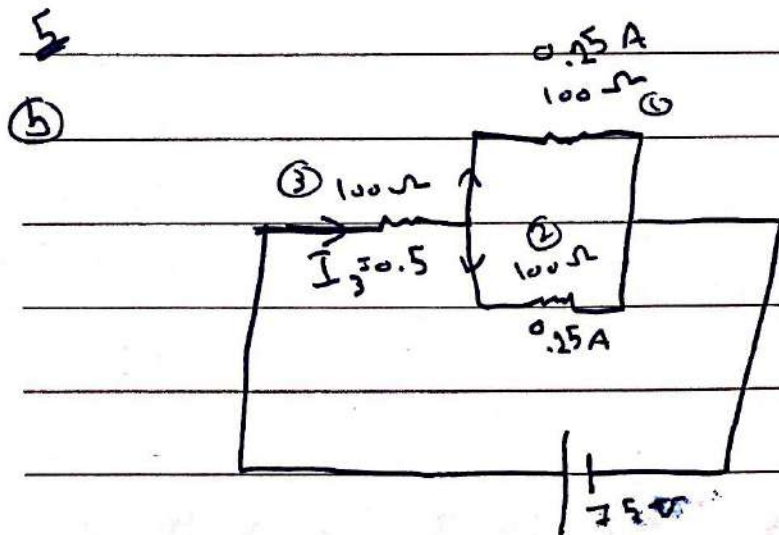

$$(1,2) \Rightarrow \frac{1}{R_p} = \frac{1}{100} + \frac{1}{100} \Rightarrow R_p = 50 \Omega$$

$$(R_p, 3) \Rightarrow R_s = 100 + 50 = 150 \Omega$$

$$I_{\text{total}} = \frac{V_{\text{total}}}{R_{\text{total}}} = \frac{75}{150} = 0.5 \text{ A}$$

$$P_1 = I^2 R_1 = (0.25)^2 \times 100 = 6.25 \text{ W}$$

$$P_2 = I^2 R_2 = (0.25)^2 \times 100 = 6.25 \text{ W}$$

$$P_3 = I^2 R_3 = (0.5)^2 \times 100 = 25 \text{ W}$$

$$\underline{15} \quad R_1, R_2 \Rightarrow R_s = 690 \, \Omega, \quad R_p = 150 \, \Omega$$

$$690 = R_1 + R_2 \quad \text{--- (1)}$$

$$\frac{1}{150} = \frac{1}{R_1} + \frac{1}{R_2} \quad \text{--- (2)}$$


$$\frac{1}{150} = \frac{1}{R_1} + \frac{1}{690 - R_1}$$

$$\frac{1}{150} = \frac{R_1 + 690 - R_1}{R_1(690 - R_1)}$$

$$\frac{1}{150} = \frac{690}{690R_1 - R_1^2}$$

$$R_1^2 - 690R_1 + 103500 = 0$$
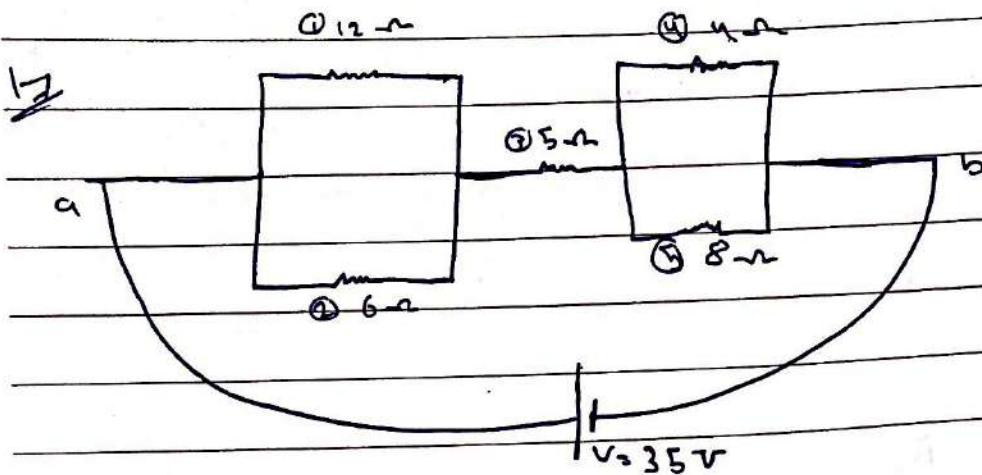
$$R_1 = 469.5 \, \Omega \quad R_2 = \del{220.5} 220.5 \, \Omega$$




$$(12, 6) \rightarrow P \Rightarrow \frac{1}{R_{P1}} = \frac{1}{12} + \frac{1}{6} \Rightarrow R_{P1} = 4\Omega$$

$$(4, 8) \rightarrow P \Rightarrow \frac{1}{R_{P2}} = \frac{1}{4} + \frac{1}{8} \Rightarrow R_{P2} = \frac{8}{3}\Omega$$

$$(R_{P1}, R_{P2}, 5) \rightarrow S \Rightarrow R_S = 4 + 5 + \frac{2}{3} = 11.6\Omega$$
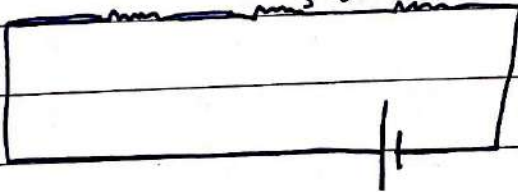
$$R_{P1} = 4\Omega \quad R_{P2} = \frac{8}{3}\Omega$$




$$I_{total} = \frac{35}{11.6} = 3A$$

$$V_{R_{P1}} = 3 \times 4 = 12 = V_1 = V_2$$

$$I_1 = \frac{12}{12} = 1A, \quad I_2 = \frac{12}{6} = 2A$$

$$\Rightarrow V_{R_{P2}} = 3 \times \frac{8}{3} = 8V = V_4 = V_5$$
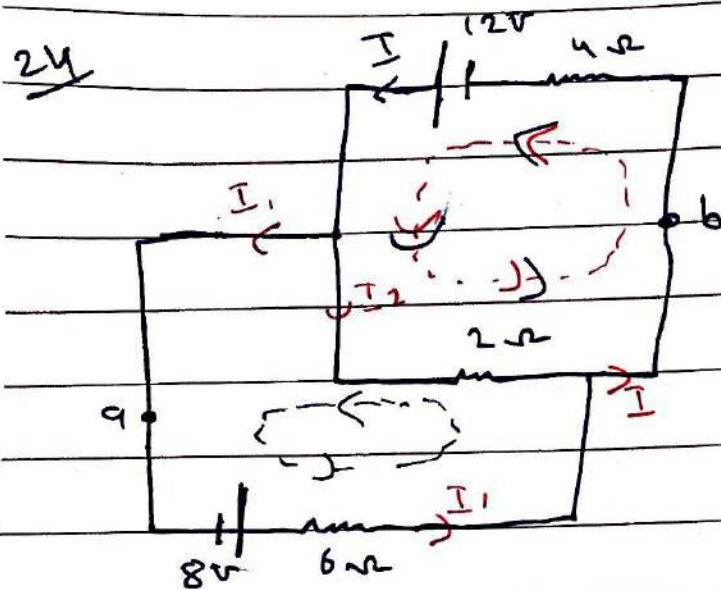
$$I_4 = \frac{8}{4} = 2A, \quad I_5 = \frac{8}{8} = 1A$$



$$I = I_1 + I_2$$

$$-4I + 12 - 2I_2 = 0$$

$$-4(I_1 + I_2) + 12 - 2I_2 = 0$$

$$-4I_1 - 6I_2 + 12 = 0$$

$$2I_2 + 8 - 6I_1 = 0$$

$$(-6I_1 + 2I_2 + 8 = 0) \times 3$$

$$-18I_1 + 6I_2 + 24 = 0$$

$$-4I_1 - 6I_2 + 12 = 0$$

$$-22I_1 + 36 = 0 \Rightarrow I_1 = 1.6 \text{ A}$$

$$-4 \times 1.6 - 6I_2 + 12 = 0 \Rightarrow I_2 = 0.93 \text{ A}$$

$$I = I_1 + I_2 = 1.6 + 0.93 = 2.53 \text{ A}$$

$$V_{ab} = V_a - V_b$$

$$V_a - 2I_2 = V_b$$

$$V_a - 2 \times 0.93 = V_b$$

$$V_a - V_b = 1.86 \text{ V}$$